Nama: Riyan Sutantio Bangkit Nugroho

NIM : L200180180

## Praktikum 6

## Percobaan 5

Fungsi Boolean : F = A'B' + A'CD + AC'D + ABC' + B'CD'

## Rangkaian:

